

THE UNITED REPUBLIC OF TANZANIA  
NATIONAL EXAMINATIONS COUNCIL  
CERTIFICATE OF SECONDARY EDUCATION EXAMINATION

031/2B

PHYSICS 2B  
ACTUAL PRACTICAL B  
(For Both School and Private Candidates)

Time: 2:30 Hours

Wednesday, 16<sup>th</sup> November 2016 a.m.

Instructions

1. This paper consists of two (2) questions. Answer all the questions.
2. Calculations should be clearly shown.
3. Marks for questions are indicated at the end of each question.
4. Calculators and cellular phones are not allowed in the examination room.
5. Write your Examination Number on every page of your answer booklet(s).
6. Use  $\pi = 3.14$ .



1. You are provided with a knife edge, a meter rule whose mass  $m$  is about 70g and an unknown mass  $M$  of the solid.

- (a) Balance the meter rule graduated face upwards on the knife edge with the solid of unknown mass  $M$  suspended at a distance  $d$  of 10cm from the zero end of the meter rule as shown in Figure 1.

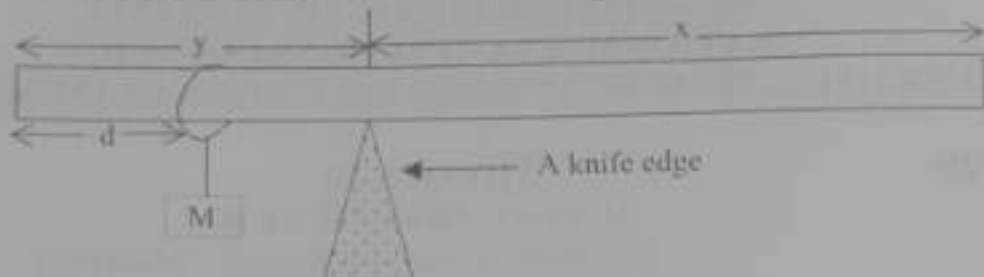


Figure 1

- (b) Measure and record the distance  $x$  and  $y$  where  $y$  is the distance of the knife edge from the zero end of the meter rule.
- (c) Repeat procedure (a) and (b) for values of  $d$  equal to 15cm, 20cm, 25cm, 30cm and 35cm.
- (d) Tabulate your results including the values of  $(x-y)$  and  $(y-d)$ .
- (e) Plot a graph of  $(x-y)$  against  $(y-d)$ .
- (f) Determine the slope,  $s$ , of your graph.
- (g) Calculate the mass  $M$  of the solid from the equation,  $\frac{sm}{2} = M$ , where  $m$  is the mass of the meter rule.
- (h) What is the aim of this experiment?
- (i) Use the mass of the solid obtained in 1 (g) to find the relative density of the solid assuming that when the solid is immersed in water its mass becomes 42.5g, and state the principle applied in this case.
- (j) State any possible source of error. (25 marks)
2. The aim of this experiment is to determine the resistivity of a wire  $Z$  provided by using a meter bridge.

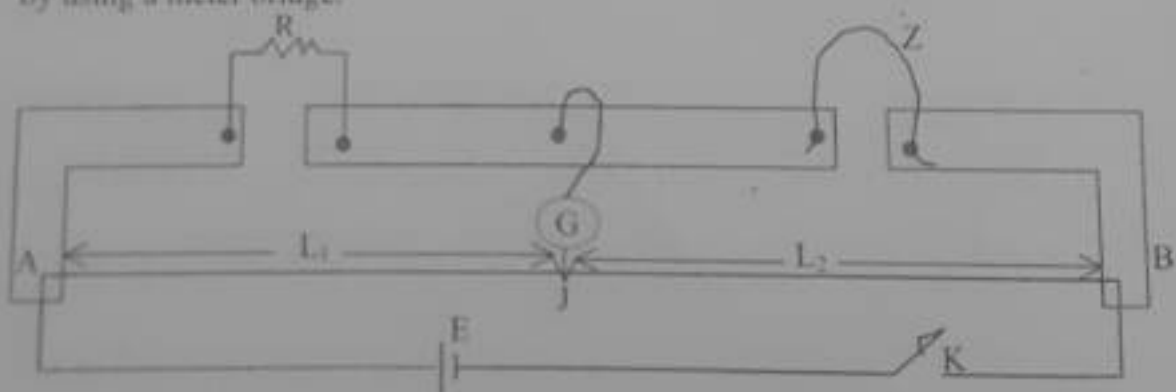


Figure 2

- (a) Connect the given apparatus as shown in Figure 2 with ends of the wire  $Z$  connected at the right hand gap of the meter bridge.

- (b) Find the balancing point of the meter bridge circuit with the jockey  $J$  when the value of the known resistance  $R$  is  $1\Omega$ .
- (c) Read and record length  $L_1$  and  $L_2$  as indicated in the diagram in Figure 2.
- (d) Repeat the procedures (a) to (c) for values of  $R = 2\Omega, 3\Omega, 5\Omega$  and  $8\Omega$ . Record their corresponding length  $L_1$  and  $L_2$ .
- (e) Record your results in a suitable table including the values of  $\frac{L_1}{L_2}$ .
- (f) Plot a graph of  $R$  against  $\frac{L_1}{L_2}$ .
- (g) Determine the gradient  $G$  of your graph.
- (h) Measure the length  $L$  of the wire  $Z$  given and its diameter  $D$ .
- (i) Calculate the resistivity of the wire  $Z$  from the expression  $L = \frac{\pi D^2 G}{4\rho}$ .

(25 marks)